


Q1

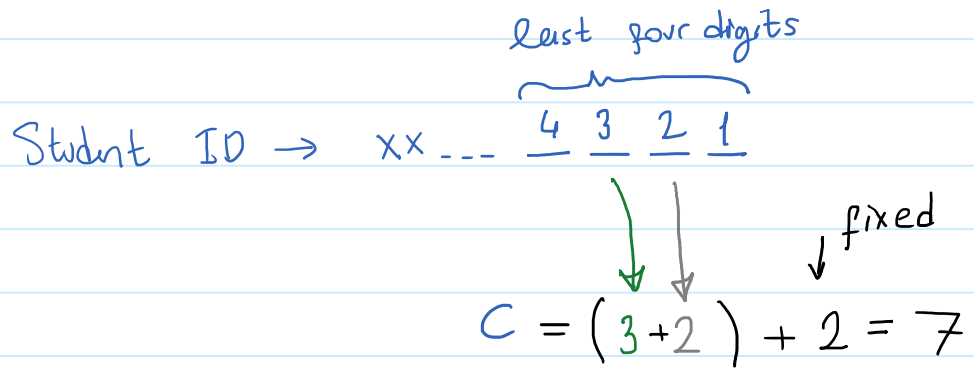

C = ? Write only the answer, no calculations!!!

Q2

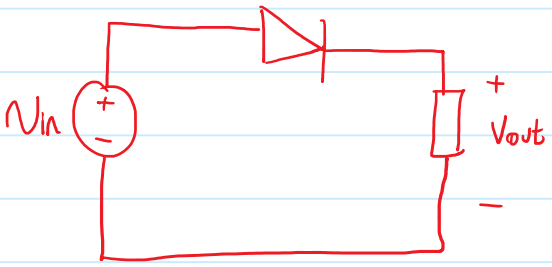

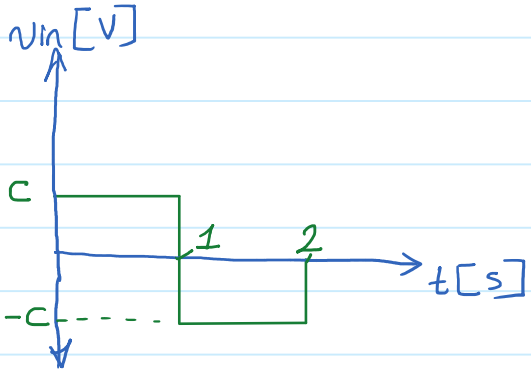

Average value of the input signal $\Rightarrow \frac{1}{T}\int_0^T v_{in}\,dt = \frac{1}{2}(C - C) = 0$

Calculate the average value of v_{out} in the range $[0,2]$.

(Hint : First plot v_{out} and then calculate $\frac{1}{2}\int_0^2 v_{out}\,dt$)

