

Q1

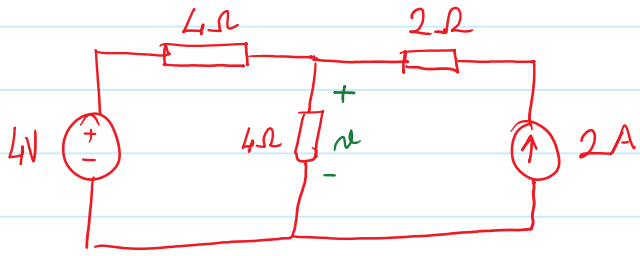

v=? Use superposition

Answer : $v_1 + v_2 = 2 + 4 = 6V$


Q2

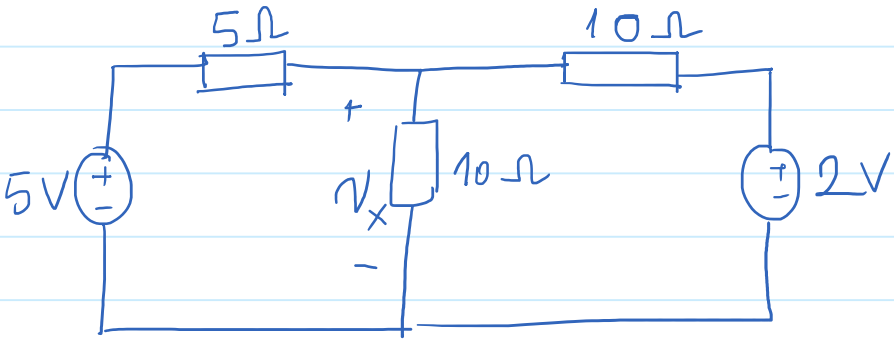

Use source transformation to calculate v_x.


Answer : $v_x = 15V$

Q3

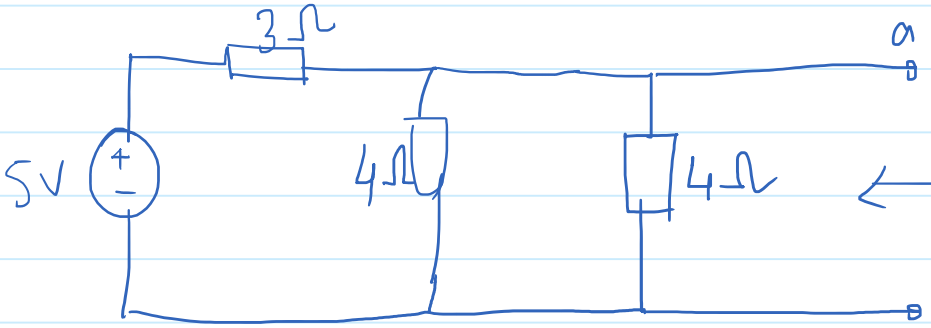


find the Thevenin Cirait

Answer:

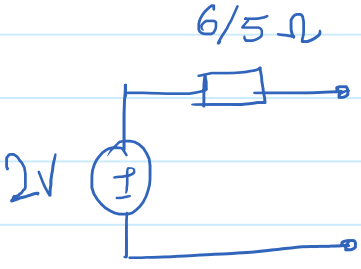

Q4

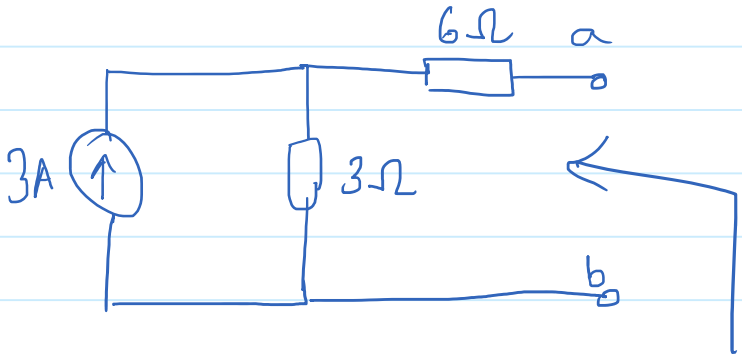

Find the equvalent Northon Circuit

