

Q1

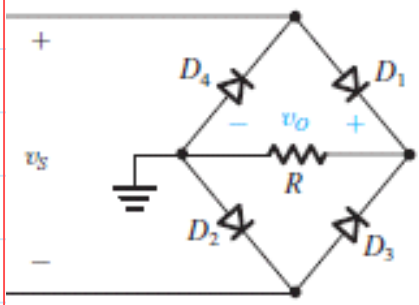


Draw the transfer characteristic of the given full-wave rectifier.


Answer:

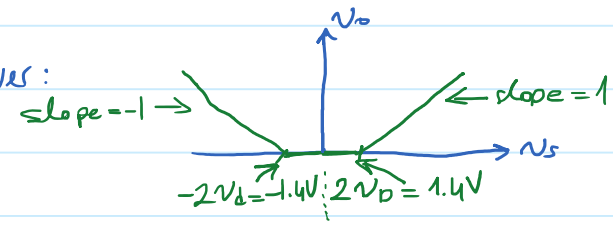


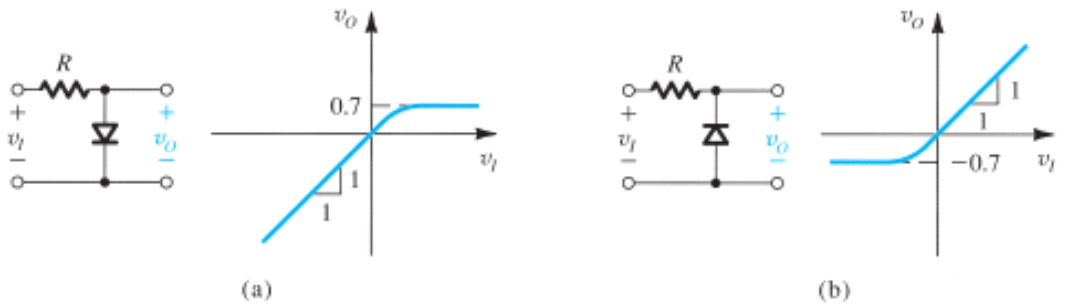Q2

For the given circuits draw the transfer characteristics.



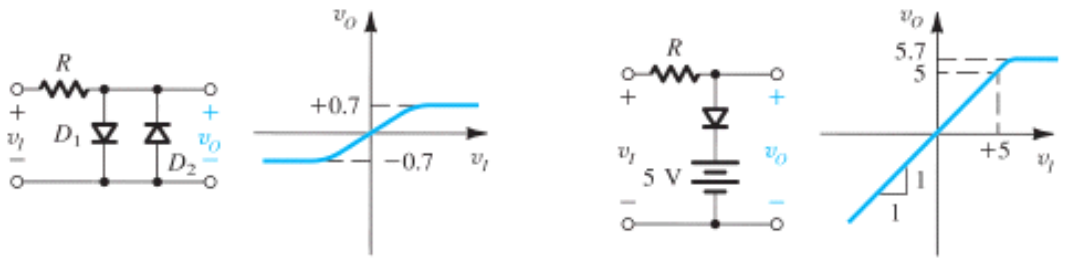

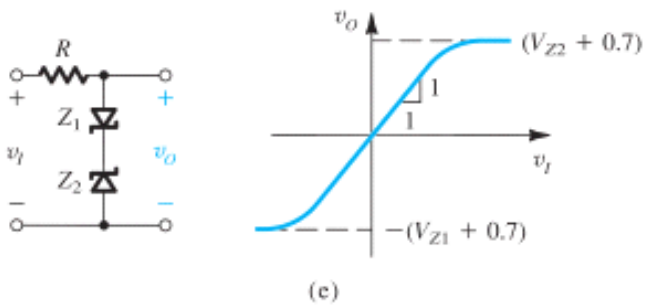

Q3

4.90 Sketch and clearly label the transfer characteristic of the circuit in Fig. P4.90 for $-15\,\text{V} \le v_I \le +15\,\text{V}$. Assume that



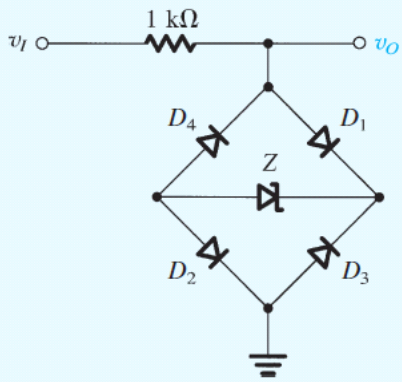



Figure P4.90

Answer:

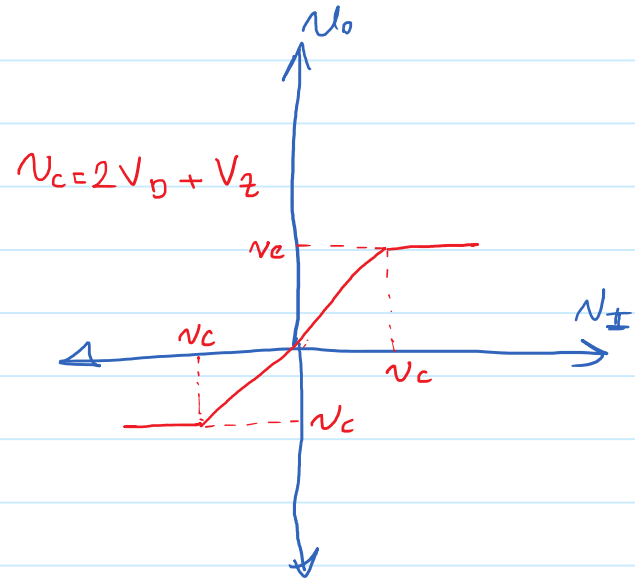

Q4

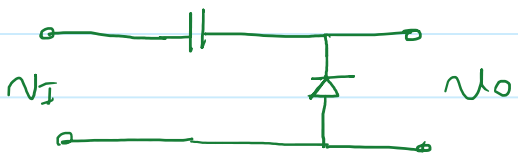

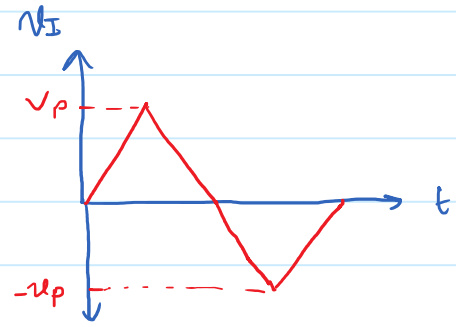

Plot t vs v_o. (Assume diode is ideal)

Answer:

