


Q1

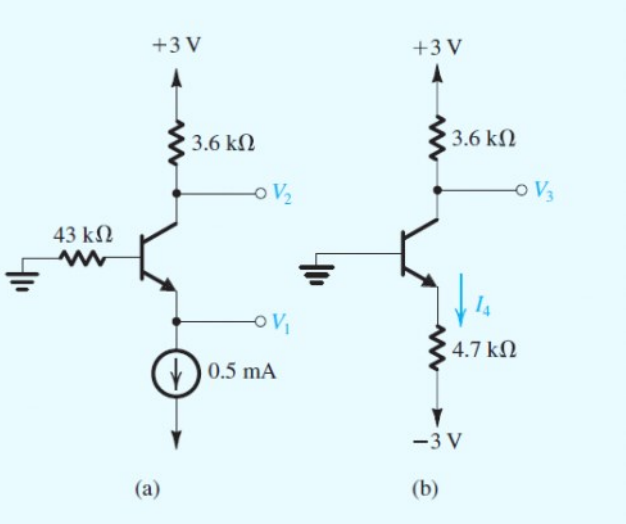6.61 For the circuits in Fig., find values for the labeled node voltages and branch currents. $\beta = 100$.




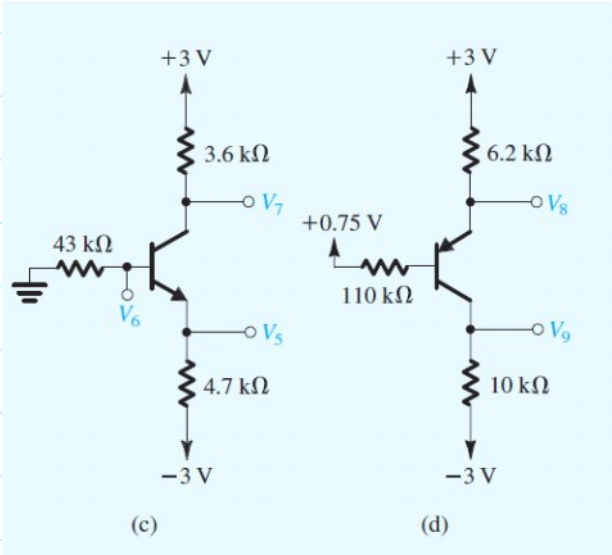


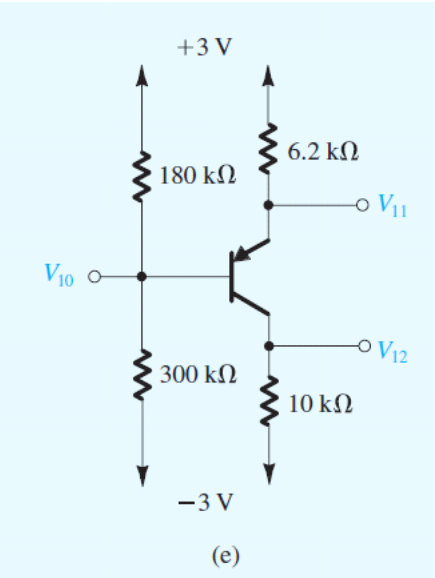

Q2

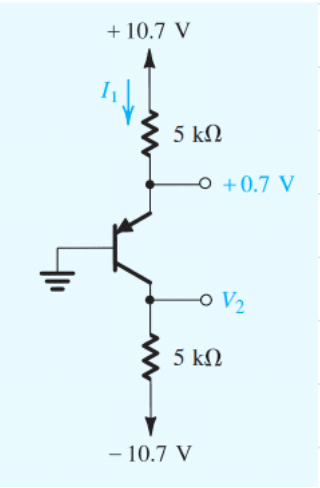
6.28 For the circuits in Fig. P6.28, assume that the transistors have very large β. Some measurements have been made on these circuits, with the results indicated in the figure. Find the values of the other labeled voltages and currents.



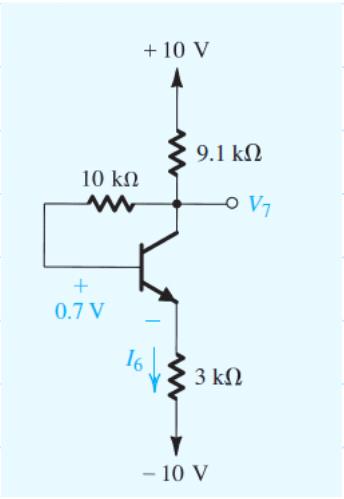

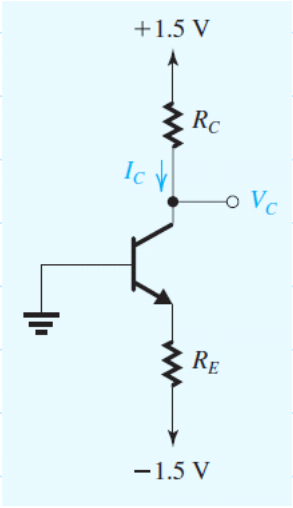Q3

D 6.34 Design the circuit in Fig. P6.34 to establish $I_C =$ 0.2 mA and $V_C = 0.5$ V. $\beta = 100$.



Q4

6.51 The transistor in the circuit of Fig. P6.51 has a very high β. Find V_E and V_C for V_B (a) +2.0 V, (b) +1.7 V, and (c) 0 V.

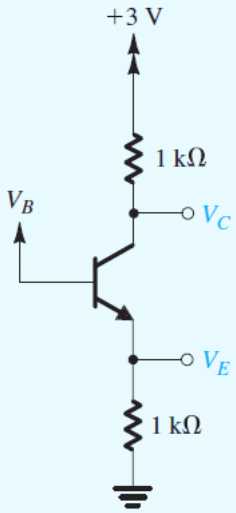


Figure P6.51