

EE232.1/2032.1 - LAB EXPERIMENT 2 - QUIZ

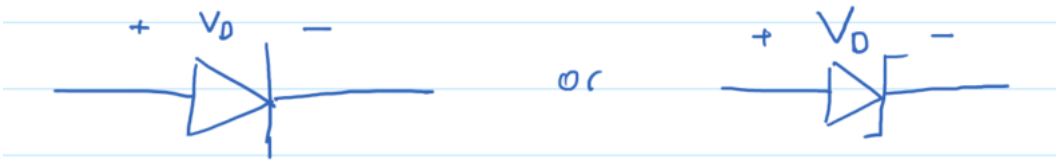

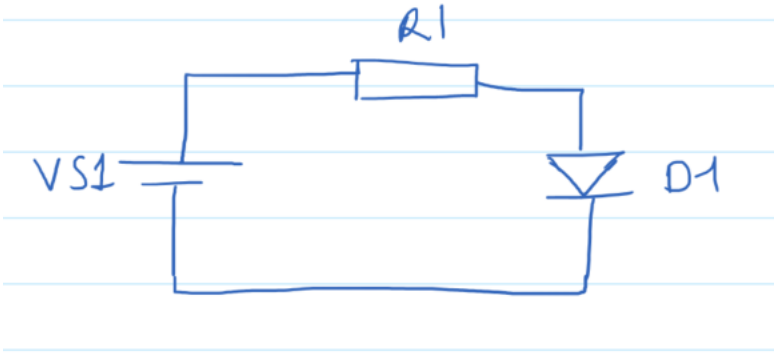1. **Q: If the voltage across a diode (V_D) is known to be negative, which of the following may be TRUE?**
    a. The diode is forward biased.
    b. The diode is reverse biased.
    c. The diode is in break-down region.



2. **Q: For the given circuit, what is going to be the relation between resistor R1 and diode D1.**
    a. The resistor draws power from the diode.
    b. The current of the resistor is equal to the current of the diode.
    c. The diode increases the voltage across the resistor.
    ç. There is no relationship between them.

3. **Q: What is the main purpose of using zener diodes?**
    a. To protect a circuit from reverse currents
    b. To emit green light
    c. To obtain a constant voltage

4. **Q: Is the following statement true or false? "Under forward biasing, a zener diode acts like a normal diode."**
    a. true
    b. false