FSM WITHIN KEYPAD

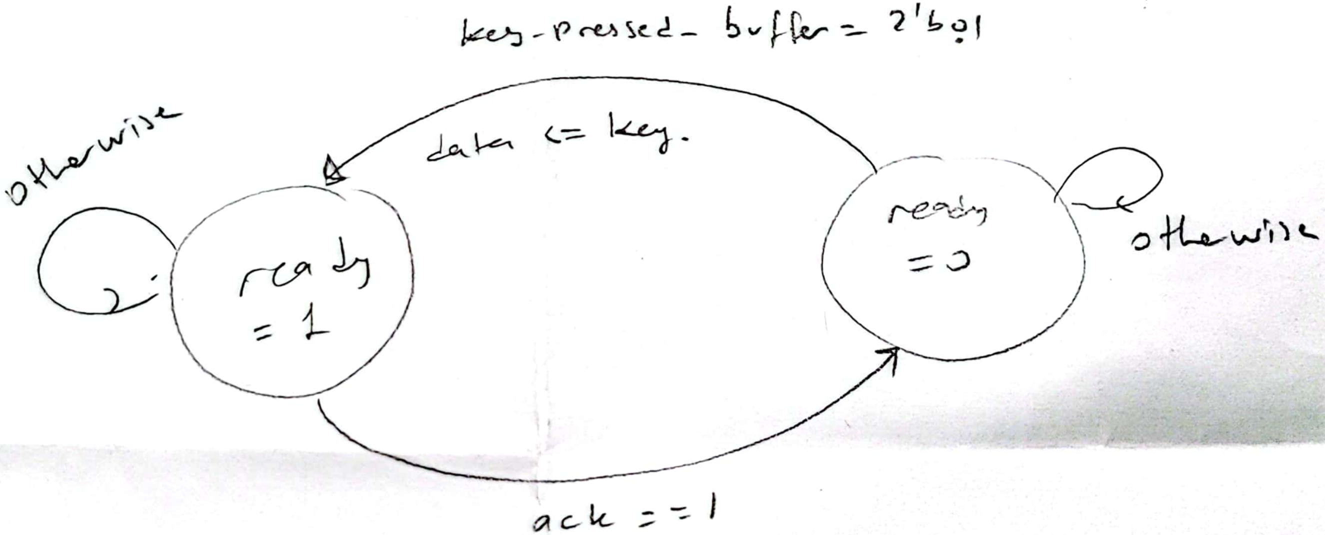
key-pressed_buffer = 2'b01
data <= key.
otherwise
ready = 1
ready = 0
otherwise
ack == 1

FSM OF TOP MODULE

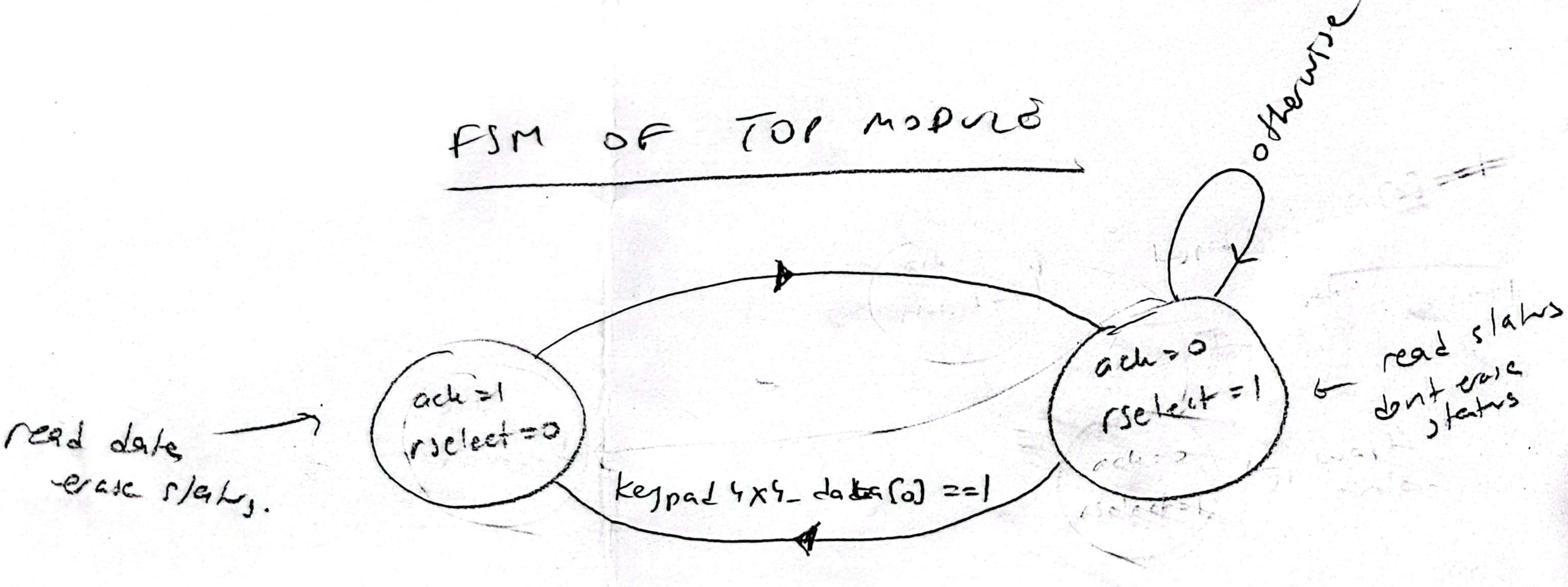
otherwise
ack = 0
rselect = 1
read status
dont erase status
ack = 1
rselect = 0
read data
erase status.
keypad4x4_data[0] == 1

lines
27-40

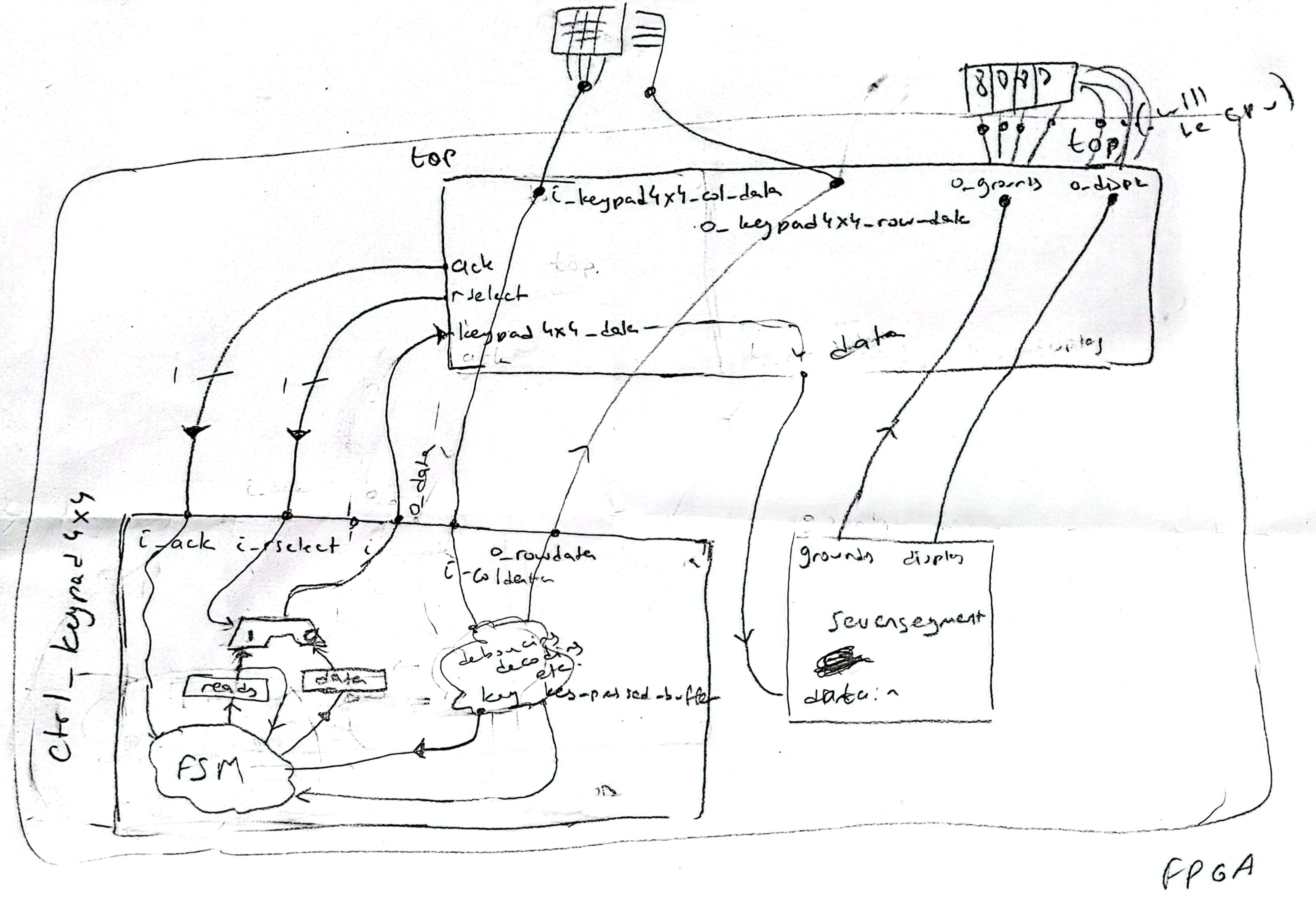
top
i_keypad4x4_col_data
o_keypad4x4_row_data
o_grounds
o_displ
top
(will be given)
ack
r_select
keypad 4x4_data
data
o_data
i_ack
i_rselect
i
o_rowdata
i_coldata
debouncing
decoding
etc.
key_kes-passed-buffer
reads
data
FSM
ctrl_keypad4x4
grounds
displays
sevensegment
data:n
FPGA